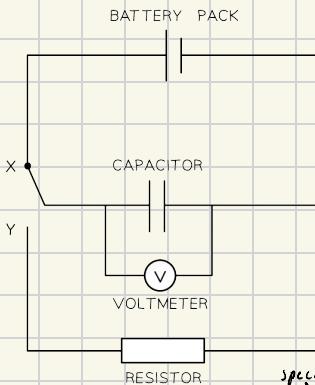


# Capacitors Required practical



Apparatus	Purpose
Switch	To switch between the charging and discharging circuit
Capacitor	To measure the capacitance
10 kΩ Resistor	To discharge the capacitor
Battery pack (power supply)	To provide the potential difference across the capacitor
Voltmeter	To measure the potential difference across the capacitor
Stopwatch	To measure the time taken for the capacitor to discharge

Resolution:

voltmeter = 0.1V

stopwatch = 0.01s

Variables:

independent = time ( $t$ )

dependent = potential difference ( $V$ )


control = Resistance of resistor  
current of circuit

Discharge

Potential difference (V)	Time (t/s)	$\ln(V)$	2nd	specified
6	0 0 0 0	1.192		$C = 1000 \mu F$
5.5	1.72 1.81 1.70 1.51	1.10		$V = 6V$
5	2.80 2.65 2.70 2.71	1.61		$R = 15 k\Omega$
4.5	4.11 4.29 4.30 4.23	1.50		$\mu = \times 10^{-6}$
4	5.48 5.36 5.15 6.00	1.34		
3.5	8.29 8.30 8.09 9.22	1.25		
3	10.26 10.06 10.65 10.31	1.1		
2.5	13.10 12.66 11.2 12.09	0.91		
2	16.92 16.23 16.91 11.33	0.69		
1.5	21.66 20.51 19.65 20.71	0.41		
1	26.11 27.05 26.98 26.92	0		
	T <sub>1</sub> T <sub>2</sub> T <sub>3</sub> mean			

$y = -0.066209830167x + 1.7$

+ Input...

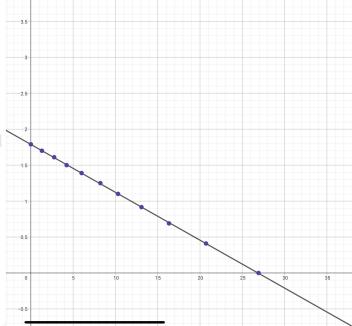

$$\frac{1}{0.0666} \times 15000 = C = 1 \times 10^{-3} F = 1021 \mu F$$

$$= \frac{1000}{2} \text{ uncertainty} = 500$$

equation:

$$I = I_0 e^{-\frac{t}{RC}}$$

$$\frac{I}{I_0} = e^{-\frac{t}{RC}}$$

$$\ln\left(\frac{I}{I_0}\right) = -\frac{t}{RC}$$

$$\ln(I) = \ln(I_0) - \frac{t}{RC}$$

errors:

systematic:

dig. voltmeter — volt till one value.

parallax error — with ammeter

Random:

resistor with large resistance — slow discharge


Safety:

- don't use a too low resistor
- don't touch while charged
- make sure no fluid touches electronics

charge

V	time
1	0
1.5	1.93
2	2.77
2.5	3.18
3	4.6
3.5	8.16
4	9.62
4.5	10.06
5	17.01
5.5	21.63
6	26.10

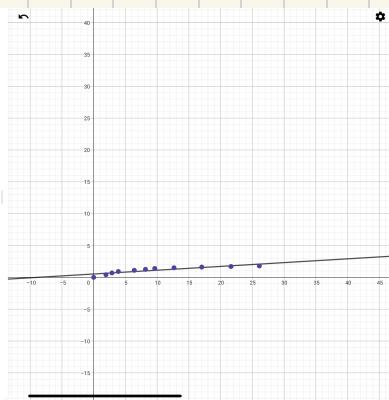f : FitLine((TableValuesP ...  
=  $y = 0.05964745076x +$   
+ Input...)



$\frac{1}{0.06} \times 15000 =$   
 $= 1.0 \times 10^{-3} F = 1.01 \mu F$   
 $\frac{1}{1000} = 1.1\% \text{ uncertainty}$

The practical went incredibly well with my accuracy below 5%. To further my experiment's accuracy I would use a stop watch with more accurate readings for more accurate time readings, as the uncertainty stems from parallax error and my reaction speed when starting/stopping the stop watch.